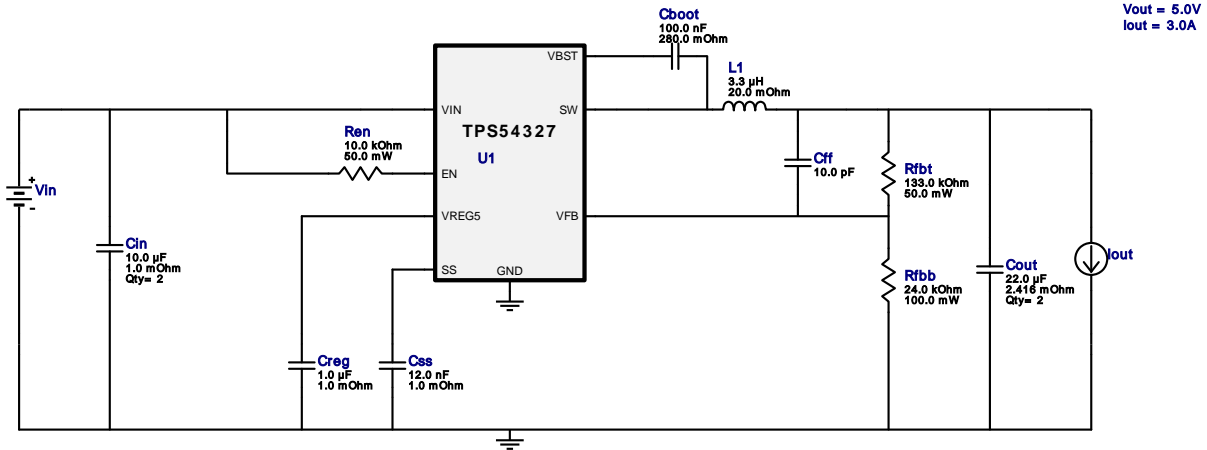



WEBENCH® Design Report







Design : 23 TPS54327DDAR
TPS54327DDAR 8V-14V to 5.00V @ 3A










Electrical BOM

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cboot	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
Cff	Kemet	C0805C100M4GACTU Series= C0G/NP0	Cap= 10.0 pF VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
Cin	MuRata	GRM32ER71J106KA12L Series= X7R	Cap= 10.0 uF ESR= 1.0 mOhm VDC= 63.0 V IRMS= 6.0 A	2	\$0.30	1210_280 15 mm ²
Cout	TDK	C3216X5R1C226M160AB Series= X5R	Cap= 22.0 uF ESR= 2.416 mOhm VDC= 16.0 V IRMS= 0.0 A	2	\$0.21	1206 11 mm ²
Creg	Kemet	C0603C105Z8VACTU Series= Y5V	Cap= 1.0 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	0603 5 mm ²
Css	MuRata	GRM033C80J123KE01D Series= X6S	Cap= 12.0 nF ESR= 1.0 mOhm VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0201 2 mm ²
L1	TDK	VLP8040T-3R3N	L= 3.3 uH 20.0 mOhm	1	\$0.22	VLP8040 113 mm ²
Ren	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
Rfbb	Yageo	RC0603FR-0724KL Series= ?	Res= 24.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm ²
Rfbt	Yageo	RC0201FR-07133KL Series= ?	Res= 133.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U1	Texas Instruments	TPS54327DDAR	Switcher	1	\$0.48	 R-PDSO-G8 55 mm²

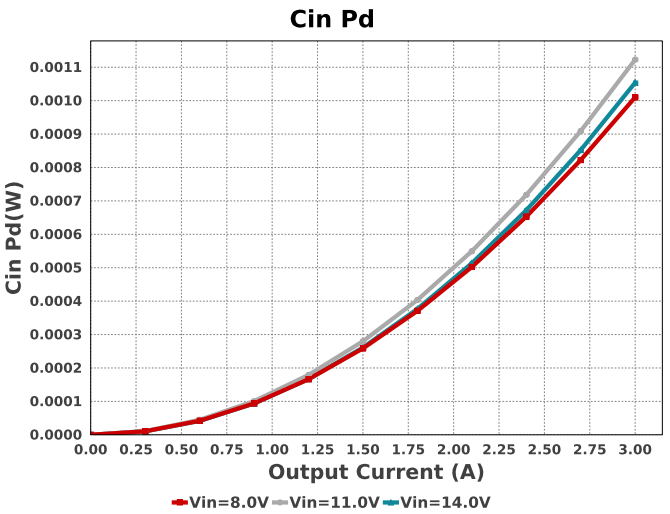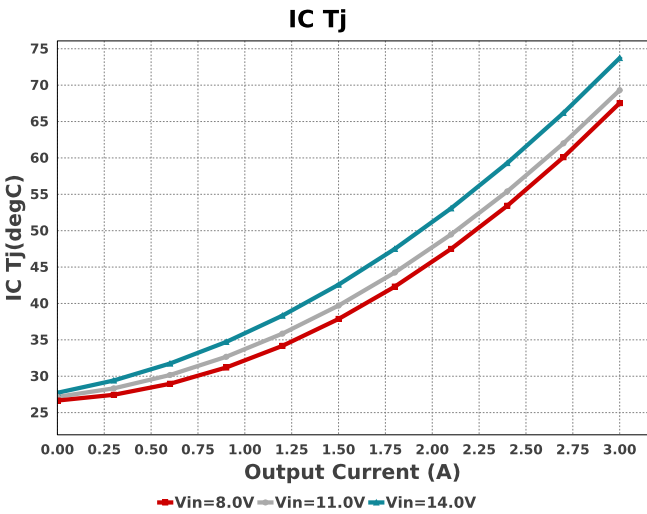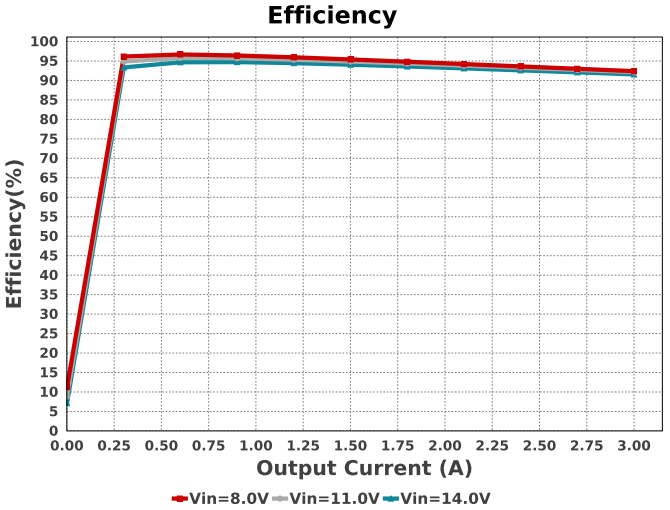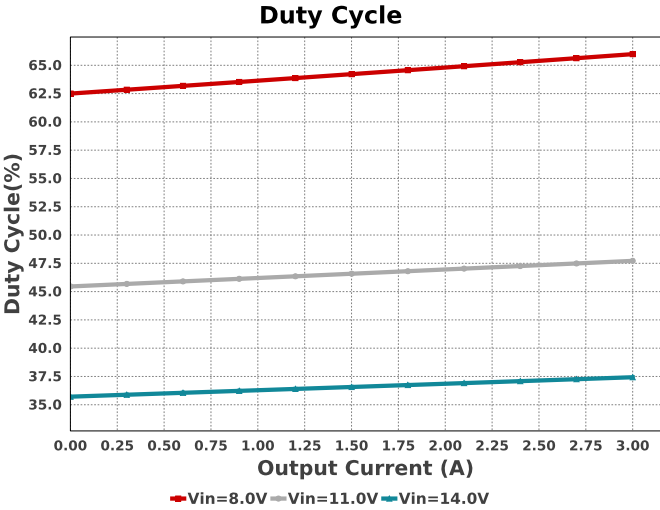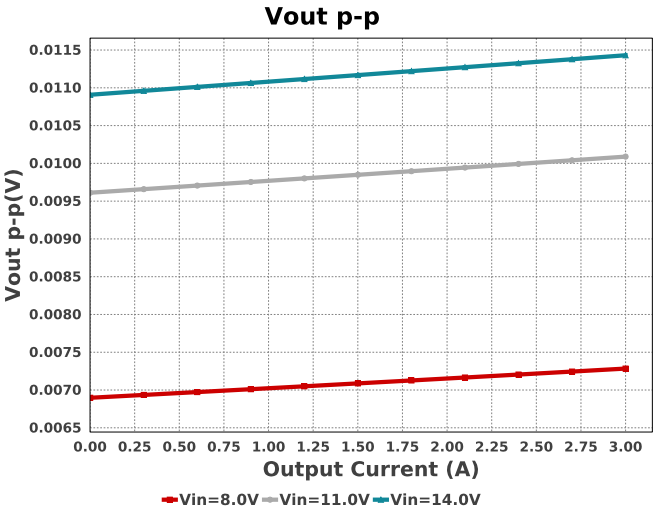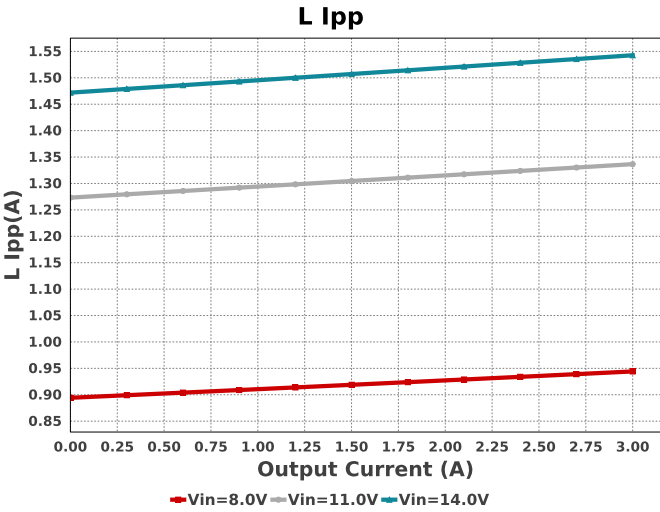

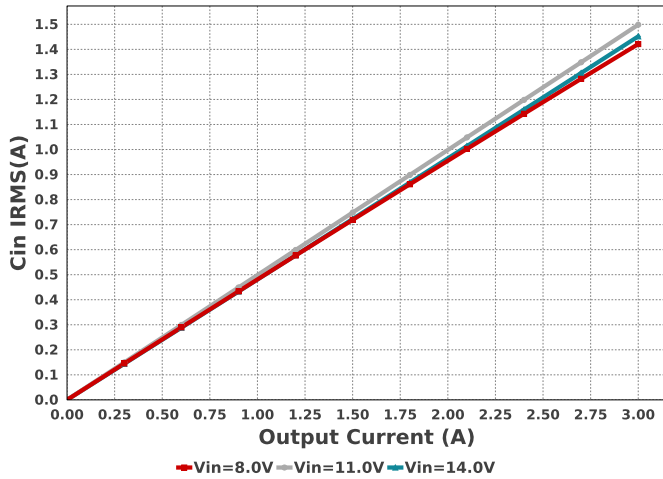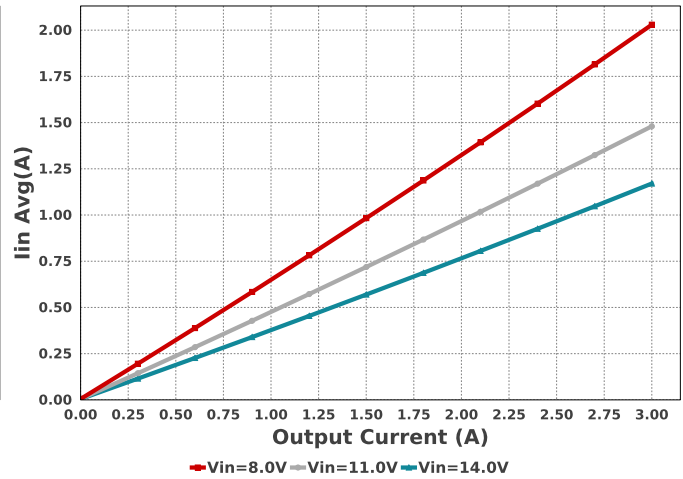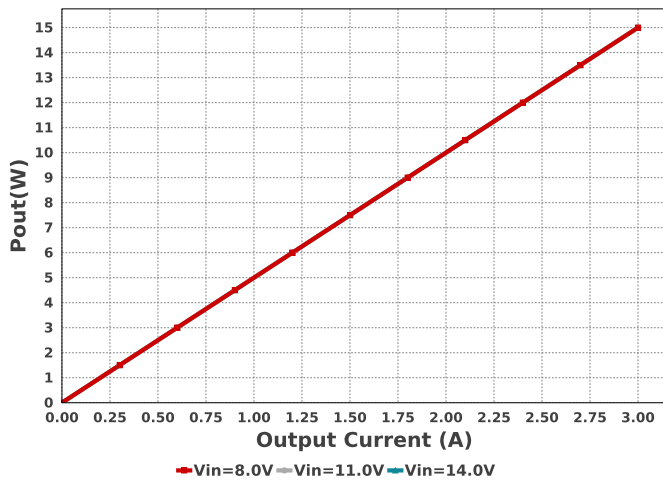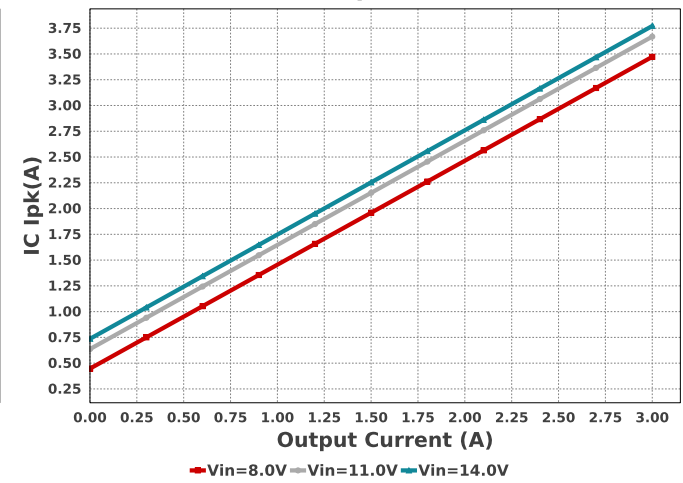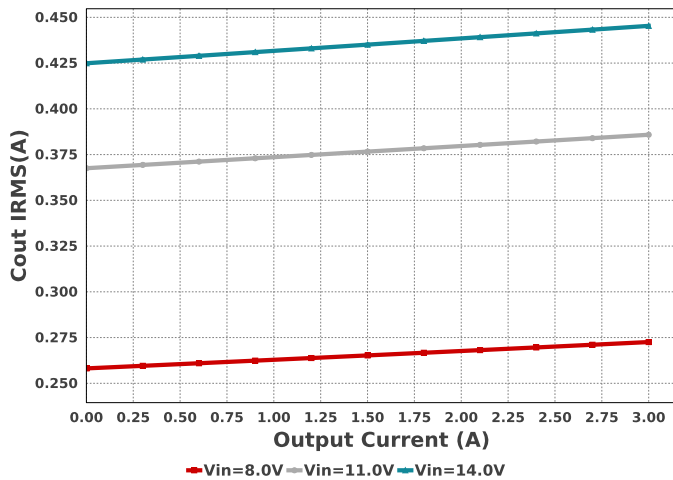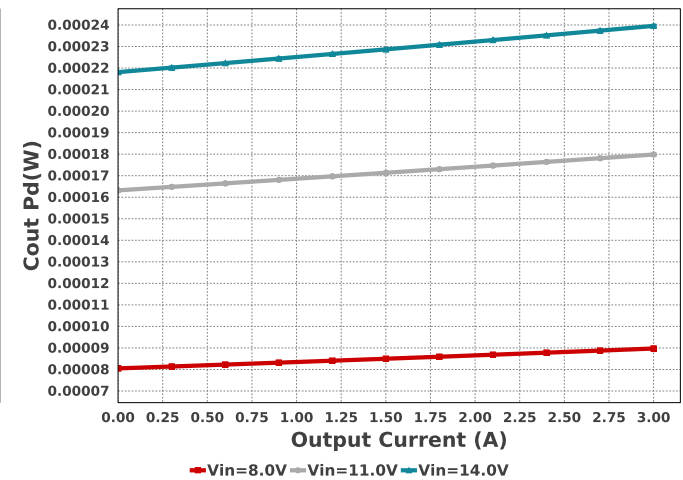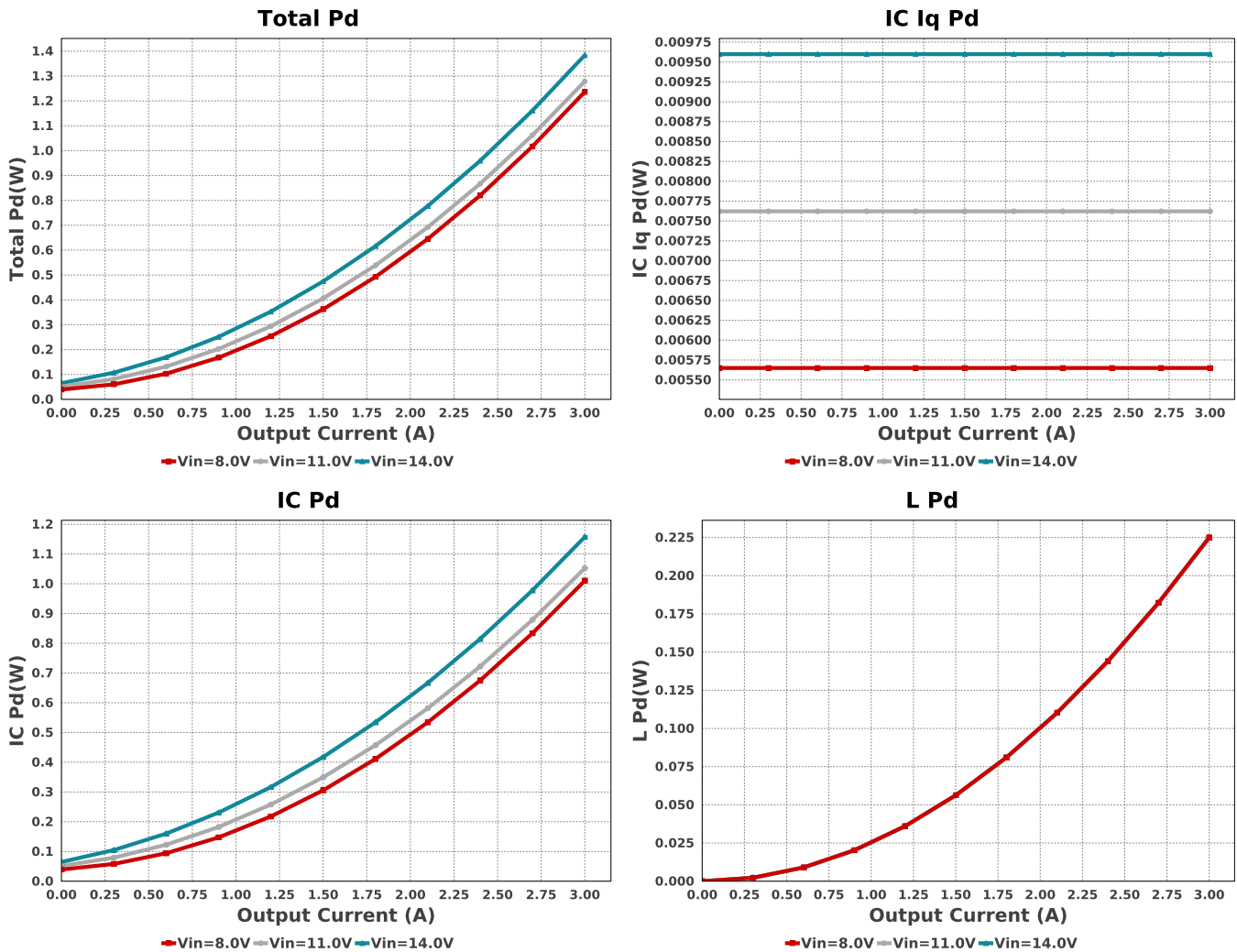Cin IRMS**Iin Avg****Pout****IC Ipk****Cout IRMS****Cout Pd**



Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.452 A	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	1.054 mW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	445.342 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	239.58 μ W	Capacitor	Output capacitor power dissipation
5.	IC Ipk	3.771 A	IC	Peak switch current in IC
6.	IC Iq Pd	9.599 mW	IC	IC Iq Pd
7.	IC Pd	1.157 W	IC	IC power dissipation
8.	IC Tj	73.727 degC	IC	IC junction temperature
9.	ICThetaJA	42.1 degC/W	IC	IC junction-to-ambient thermal resistance
10.	Iin Avg	1.17 A	IC	Average input current
11.	L Ipp	1.543 A	Inductor	Peak-to-peak inductor ripple current
12.	L Pd	225.0 mW	Inductor	Inductor power dissipation
13.	Cin Pd	1.054 mW	Power	Input capacitor power dissipation
14.	Cout Pd	239.58 μ W	Power	Output capacitor power dissipation
15.	IC Pd	1.157 W	Power	IC power dissipation
16.	L Pd	225.0 mW	Power	Inductor power dissipation
17.	Total Pd	1.384 W	Power	Total Power Dissipation
18.	BOM Count	13	System	Total Design BOM count
19.	Duty Cycle	37.432 %	Information	Duty cycle
20.	Efficiency	91.554 %	System	Steady state efficiency
21.	FootPrint	249.0 mm ²	Information	Total Foot Print Area of BOM components
22.	Frequency	661.741 kHz	System	Switching frequency
23.	Iout	3.0 A	Information	Iout operating point
24.	Mode	CCM	System	Conduction Mode

#	Name	Value	Category	Description
25.	Pout	15.0 W	System Information	Total output power
26.	Total BOM	\$1.79	System Information	Total BOM Cost
27.	Vin	14.0 V	System Information	Vin operating point
28.	Vout	5.0 V	System Information	Operational Output Voltage
29.	Vout Actual	5.004 V	System Information	Vout Actual calculated based on selected voltage divider resistors
30.	Vout Tolerance	3.573 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
31.	Vout p-p	11.431 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	3.0	Maximum Output Current
SoftStart	5.0 ms	Soft Start Time (ms)
VinMax	14.0	Maximum input voltage
VinMin	8.0	Minimum input voltage
Vout	5.0	Output Voltage
base_pn	TPS54327	Base Product Number
source	DC	Input Source Type
Ta	25.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 8.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

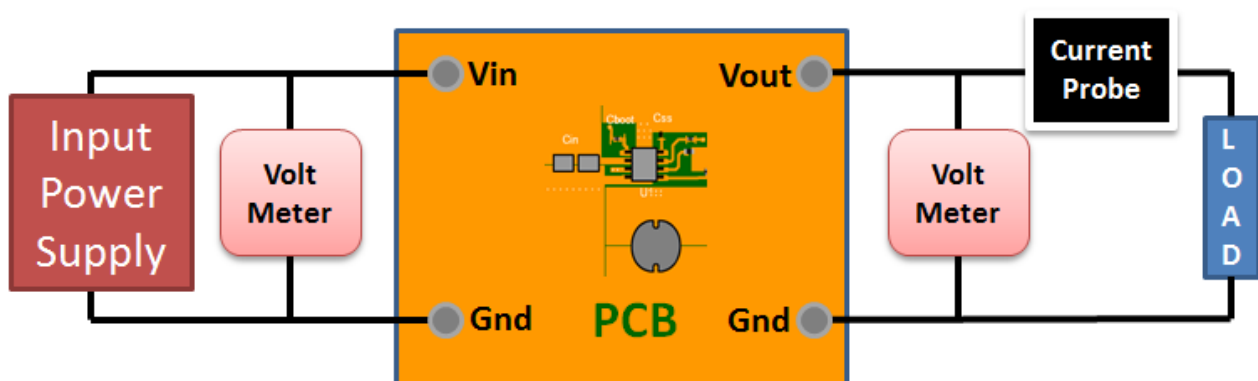

Design Assistance

1. Master key : 3A09369785B968091A003B956300BD89[v1]
2. **TPS54327** Product Folder : <http://www.ti.com/product/TPS54327> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.